

VERILOG HDL

(and C)

Some Reference Material

The following are suggested reading..

<http://engnet.anu.edu.au/DEcourses/engn3213/Documents/VERILOG/>

- **VerilogIntro.pdf** - Very simple introduction which emphasises the ground rules for good coding style
- **verilog-tutorial.pdf** - Another very simple introduction which introduces some other things but is no good on coding style
- **coding_and_synthesis_with_verilog.pdf** - explains ways to build some common circuits
- **VerilogTutorial.pdf** - a VERILOG reference with lots of useful information
- **cummings-nonblocking-snug99.pdf** - There are several other useful articles by Cummings eps. Finite State Machines in VERILOG.

Some Reference Material (ctd)

- **1996-CUG-presentation_nonblocking_assigns.pdf** - A discussion about blocking and non-blocking assignments but mostly for simulation. An interesting discussion about how to simulate inertial and transport delays in real hardware using VERILOG.
- **vlogref.pdf** - Cadence VERILOG compendium.. heaps of reference material
- **verilogSlides.pdf** - some of this lecture's slides
- **Beware of some inconsistencies and note those in the hardware blocks of MU0!**

How To Represent Hardware?

Hardware definition language provides a way of describing and documenting hardware so that

- You can read it again later
- Someone else can read and understand it
- It can be simulated and verified
- It may be synthesised into gates
- It can be shipped and you can make money

Ways to represent hardware

- Schematics
- Write a NETLIST
- Write primitive Boolean equations
- Use **Hardware Description Language**

What are Hardware Description Languages (HDLs)?

- Textual representation of a logic design but has various levels of **abstraction**
- **Not programming languages** **YOU MUST MAKE THE CONCEPTUAL LEAP**
- Similar development chain
 - Compiler → assembly code → binary machine code
 - Synthesis tool: HDL source → gate-level specification → hardware

Why use HDLs?

- Easier to make system abstractions (VIZ the **combinational** and **sequential logic** abstractions)
- Easy to write and edit
- Compact
- Don't have to follow wires on a schematic
- Easy to analyse
- Why not to use an HDL
 - To avoid understanding the hardware
 - A schematic can be a complex work of art... **but not if you do a proper RTL design**

HDL History

- 1970s: First HDLs
- Late 1970s: VHDL
 - VHDL = VHSIC HDL = Very High Speed Integrated Circuit HDL
 - VHDL inspired by programming languages of the day (Ada)
- 1980s:
 - Verilog first introduced
 - Verilog inspired by the C programming language
 - VHDL standardized

HDL History

- 1990s:
 - Verilog standardized (Verilog-1995 standard)
- 2000s:
 - Continued evolution (Verilog-2001 standard)
- Both VHDL and Verilog evolving, still in use today
- ICARUS Verilog needs plenty of Verilog-2001 compliance - work in progress.

About Verilog...

- A surprisingly big language
 - lots of features for simulation and synthesis of hardware.
- **We are going to learn a focussed subset of VERILOG**
 - We will use it at a level appropriate for computer design
 - Focus on synthesisable constructs
 - Initially restrict some features just because they are not necessary
 - **If you haven't seen it in lectures, ask me before you use it**

Why an HDL is not a Programming Language

- In a program, we start at the beginning (e.g. 'main'), and we proceed sequentially through the code as directed
- The program represents an algorithm, a step-by-step sequence of actions to solve some problem

```
for (i = 0; i<10; i=i+1) {  
    if (newPattern == oldPattern[i]) match = i;  
}
```

- Hardware is all active at once; there is no starting point

What do you really have to know to understand and use VERILOG?

- **VERILOG can be for SYNTHESIS or for SIMULATION: you must learn to distinguish them**
- **SYNTHESISABLE VERILOG runs CONCURRENTLY in hardware (C.F. C language)**
- **VERILOG has some basic abstractions:**
 - 1. COMBINATIONAL and SEQUENTIAL**
 - 2. WIRES and REGS (not important but basic)**

What are the usual problems of VERILOG that you need to look out for?

- You are breaking with the **COMBINATIONAL / SEQUENTIAL** paradigm

- Your code is poorly synthesisable: Two ways:
 1. You are using simulation-only constructs in your code for synthesis.

 2. **YOUR CODE IS FOR SYNTHESIS BUT TRANSLATES BADLY INTO HARDWARE - THE USUAL PROBLEM**


WIRES and REGS

- Variables in VERILOG are either **WIRES** or **REGS**
- **Neither of these is like a variable in C**
- **WIRES**
 - A **WIRE** is a through-connection within or to a module. The input and output ports are **WIRES**. **ASSIGNS** assign to **WIRES**
- **REGS**
 - The combinational and sequential paradigms in terms of **ALWAYS** blocks imply a **persistence to the variables they assign to**
 - **Example: the variables on the left hand sign of statements inside ALWAYS blocks are REGS**
 - **REGS have persistence and store VALUES from one event to the next**
 - **REGS are not registers in the electronic sense**


WIRES and REGS




Circuit Schematic

 

VERILOG

 

Verilog Program Structure

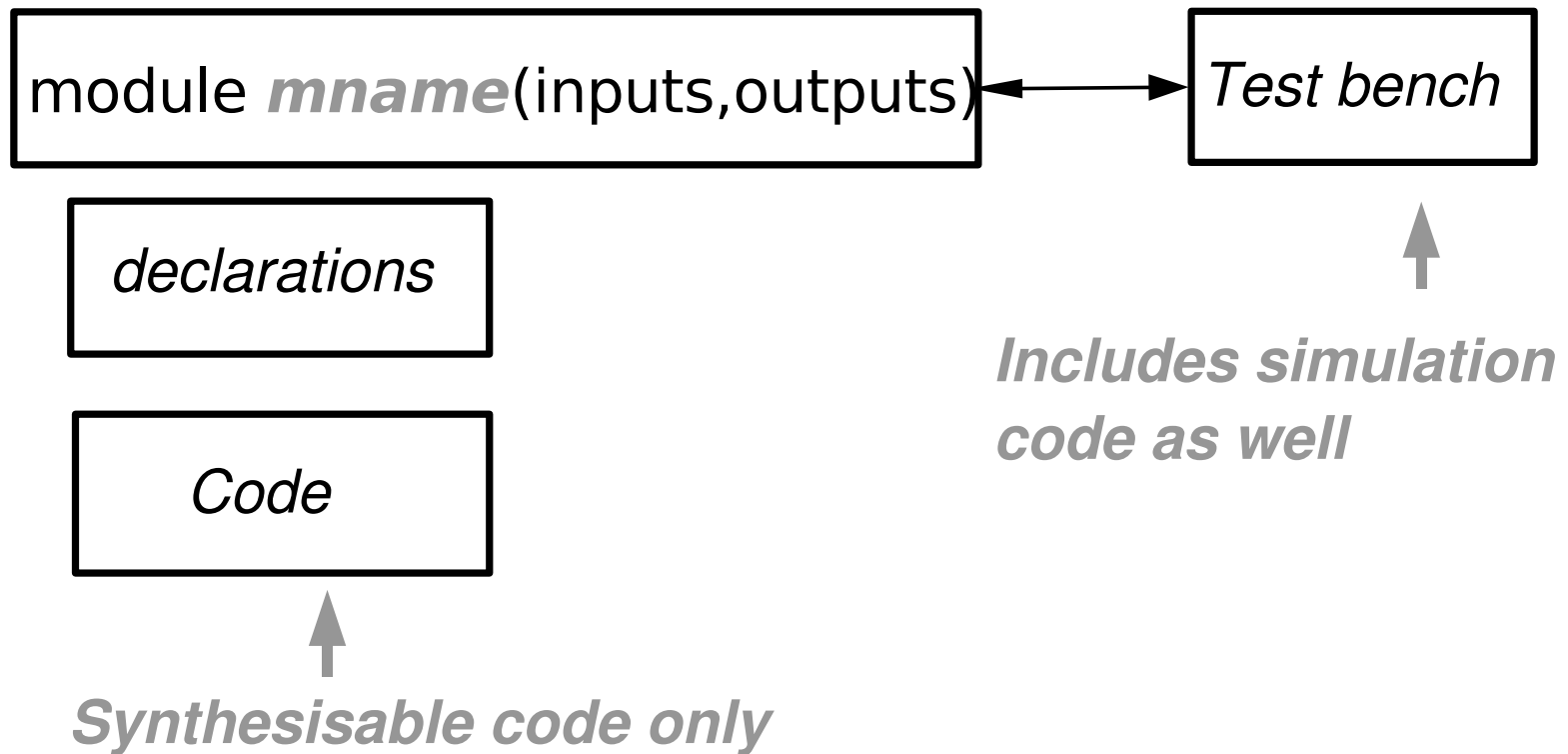

Modelling sequential and combinational circuits

```
/**
always @(posedge clk or A) begin

//Non-blocking IO
    X <= Y;
    Y <= A;
end
```

Sequential code
assignment at
the posedge clk


```
/**
always @(A or B) begin

//Blocking IO
    D = B;
    C = A;
end
```

Combinational code
All values settle,
clock period >> settling time


VERILOG by example: MULTIPLEXER (combinational)
 
```
module mux(sel, a, b, c);  
  input a;  
  input b;  
  input sel;  
  output c;  
  reg c;  
  always@(a or b or sel)  
    if (sel == 1'b1)  
      c = a;  
    else  
      c = b;  
  
  // c = sel ? a : b;  
  
endmodule
```



VERILOG by example: D-type Flip Flop (sequential)
 
```
module dff(clk, d, q);  
  input clk;  
  input d;  
  output q;  
  reg q;  
  always@(posedge clk)  
    q <= d;  
endmodule
```




ASSIGNS... an alternative construct for treating SIMPLE combinational circuits

```
module inv(a, y);  
    input [3:0] a;  
    output [3:0] y;  
    assign y = ~a;  
endmodule
```

```
module and8(a, y);  
    input [7:0] a;  
    output      y;  
    assign y = &a;  
endmodule;
```

Tristate Buffers

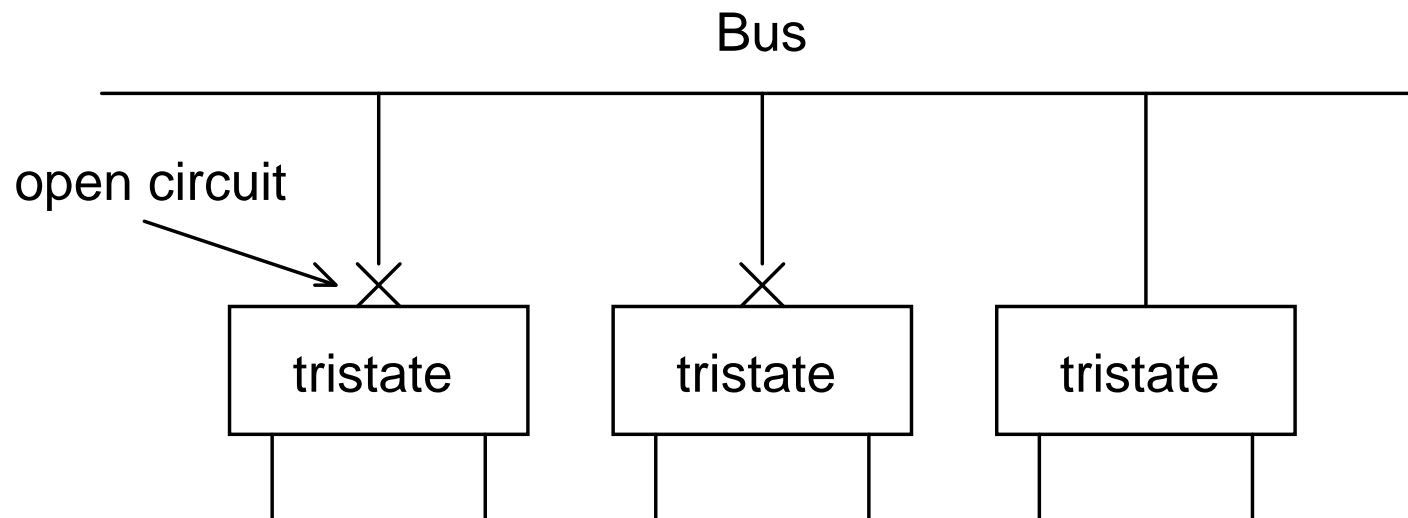- Tristate buffers are multiplexers that have the possibility of producing an open circuit output



Tristate Buffers

```
module tristate(a, en, y);  
    input [3:0] a;  
    input      en;  
    output [3:0] y;  
    assign y = en ? a : 4'bz;  
endmodule
```


```
module mux2(d0, d1, s, y);  
    input [3:0] d0, d1;  
    input      s;  
    output [3:0] y;  
    tristate t0(d0, ~s, y);  
    tristate t1(d1, s, y);  
endmodule
```

Combinational logic

```
// Using a reg
// -----
wire a,b;
reg c;
always @ (a or b)
    c = a & b;
// Using a wire
// -----
wire a,b,c;
assign c = a & b;
// using a built in primitive (without instance name)
// -----
reg a,b;
wire c;
and (c,a,b); // output is always first in the list
// using a built in primitive (with instance name)
// -----
reg a,b;
wire c;
and u1 (c,a,b); // output is always first in the list
```

Program structure example: Testing an 8 bit adder

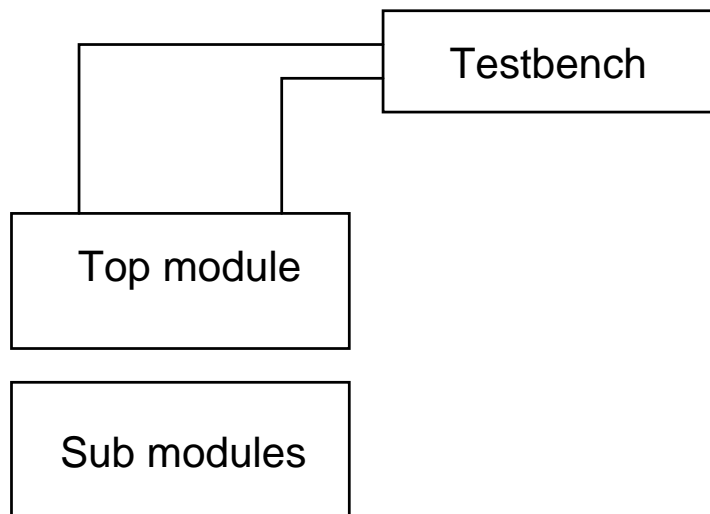- For simulation the Verilog program structure consists of synthesisable code and a testbench.



Top module

```
module adder(Xw,Yw,Sw,Cout);  
  
    input [7:0] Xw;  
    input [7:0] Yw;  
  
    output [7:0] Sw;  
    output Cout;  
  
    wire [7:0] Sw;  
  
    full_adder fa0(Xw[0],Yw[0],Sw[0],0 ,C0);  
    full_adder fa1(Xw[1],Yw[1],Sw[1],C0,C1);  
    full_adder fa2(Xw[2],Yw[2],Sw[2],C1,C2);  
    full_adder fa3(Xw[3],Yw[3],Sw[3],C2,C3);  
    full_adder fa4(Xw[4],Yw[4],Sw[4],C3,C4);  
    full_adder fa5(Xw[5],Yw[5],Sw[5],C4,C5);  
    full_adder fa6(Xw[6],Yw[6],Sw[6],C5,C6);  
    full_adder fa7(Xw[7],Yw[7],Sw[7],C6,Cout);  
  
endmodule
```

1 bit full adder

```
module full_adder(X,Y,S,Cin,Cout);  
  
  input X;  
  input Y;  
  input Cin;  
  
  output S;  
  output Cout;  
  
  assign S = (X^Y)^Cin;  
  assign Cout = ((X^Y)&Cin)|(X&Y);  
  
endmodule
```

Testbenches: A test bench for the adder

```
module TB_adder; //No inputs or outputs for a testbench

reg [7:0] X;
reg [7:0] Y;

wire [7:0] S;
wire Cout;

adder ad(X,Y,S,Cout);

initial begin
    $display("\t\ttime\t X\t Y\t S\t Cout\n");
    #1 X = 8'h0a;
    #1 Y = 8'hbb;
    #1 $display("%d\t%b\t%b\t%b\t%b\t\n", $time, X, Y, S, Cout);
end

endmodule
```

Running the simulation

```
[ggb112@localhost adder]$ more cmp.sh
```

```
#!/bin/sh  
iverilog full_adder.v adder.v TB_adder.v  
./a.out
```

```
[ggb112@localhost adder]$ sh cmp.sh
```

time	X	Y	S	Cout
3	10101011	10111011	01100110	1

Pitfalls of Treating Verilog like a Programming Language

- If you program sequentially, the synthesiser may add a lot of hardware to try to do what you say
- If you program in parallel (multiple 'always' blocks), you can get non-deterministic execution - Which 'always' happens first?

```
if(x == 1) out = 0;  
if(y == 1) out = 1; // else out retains previous state? R-S latch!
```

- You don't realize how much hardware you're specifying **e.g. $x = x + 1$ can be a LOT of hardware**
- Slight changes may suddenly make your code 'blow up'. A chip that previously fit suddenly is too large or slow

Structural vs Behavioral HDL Constructs

- Structural constructs specify actual hardware structures
 - Low-level, direct correspondence to hardware
 - Primitive gates (e.g., and, or, not)
 - Hierarchical structures via modules
- Behavioural constructs specify an operation on bits
 - High-level, more abstract
 - Specified via equations, e.g.
$$\text{out} = (a \& b) | c$$
- Not all behavioural constructs are synthesisable
 - We've already talked about the pitfalls of trying to 'program'
 - But even some combinational logic won't synthesise well
 - `out = a % b // modulo operation - what does this synthesise to?`
 - **The following are discouraged for synthesis:**
`+ ... - ... * % ... < ... <= ... < ... <= ... << ... >>`

ENGN3213 Software

Applications Places System 6:30

Index of /DEcourses/engn3213/Software/WINDOWS - Mozilla Firefox

File Edit View Go Bookmarks Tools Help

http://engnet.anu.edu.au/DEcourses/engn3213/Software/WINDOWS Go

Release Notes Fedora Project Fedora Weekly News Community Support Fedora Core 6

Index of /DEcourses/engn3213/Software/WINDOWS

Name	Last modified	Size	Description
Parent Directory	-	-	-
GTKWAVE.zip	10-Mar-2009 22:40	8.9M	
MU0.zip	11-Mar-2009 08:49	1.1M	
MU0_README	12-Mar-2009 06:18	646	
MinGW-3.0.0-1.exe	06-Mar-2009 13:42	1.3M	Minimalist C-compiler for windows
PCCOMP.zip	06-Mar-2009 13:42	1.3M	C compiler for PICOBLAZE
RUNMU0.png	12-Mar-2009 06:18	646	
WebPACK_SFD_92i.zip	06-Mar-2009 13:45	1.6G	
iverilog-0.8.6_setup.exe	06-Mar-2009 13:42	1.3M	
xapp213.zip	06-Mar-2009 13:42	1.3M	PICOBLAZE

Apache/2.2.9 (Ubuntu) PHP/5.2.6-2ubuntu4.1 with Suhosin-Patch Server at engnet.anu.edu.au Port 80

Done

ggb112@localho... Index of /DEcour... lecture5_and_6_... RSPSE Webmail -...



Example: Counter

- 3 bit asynchronously resettable counter which counts 0, 1, 2, 3, 4, 5
- External reset to start the counter
- Issues - switch debouncing?

```
[ggb112@localhost counter]$ more cmp.sh
#!/bin/sh
```

```
iverilog counter_3bit.v TB_counter_3bit.v
```

```
./a.out
```

```
[ggb112@localhost counter]$ sh cmp.sh
VCD info: dumpfile C3B.vcd opened for output.
```

time	clk	rst	count
3	1	0	0000
7	1	0	0001
11	1	0	0010
15	1	0	0011
19	1	0	0100
23	1	0	0101
27	1	0	0000
31	1	0	0001
35	1	0	0010
39	1	0	0011
43	1	0	0100
47	1	0	0101

Example: Counter

```
module counter_3bit( clk, rst, count );

input clk;
input rst;

wire rst; //not necessary but true

output [3:0] count;

reg [3:0] count; //count is assigned in ALWAYS block

// 3 bit asynchronously resettable
always @(posedge clk or posedge rst) begin
    if (rst)
        count <= 3'b0;
    else
        if (count == 3'b101)
            count <= 3'b0;
        else
            count <= count + 3'b001;
end

endmodule
```

Example: Counter

```
module TB_counter_3bit;

reg clk;
reg rst;
wire [3:0] cnt;

counter_3bit c3b(clk, rst, cnt);

initial begin
clk = 0;
rst = 1;
#1rst = 0;
$display("\t\t time \t clk \t rst \t count");
forever #2 clk = ~clk;
end

initial begin
    $dumpfile("C3B.vcd");
    $dumpvars;
end

initial begin: stopat
#50; $finish;
end

always @(posedge clk) begin
$display("%d\t %b \t %b \t %b", $time, clk, rst, cnt);
end
endmodule
```